

1. Design & Implementation of 1-bit ALU circuit (Using IC 4539B MUX)

